

Introduction

Finite state machines (FSM) are some of the many computational models that can be used to simulate sequential logic on an FPGA. FSM models can be classified into 2 categories, mealy FSM and moore FSM. Mealy FSM's outputs are determined by both the current state and current input. However, moore FSM's outputs are determined only by its current state. This lab aims to explore the implementation of a moore FSM on the NEXYS 4 DDR and its feasibility when compared to a test bench.

FSM logic

Moore FSM output is determined by its current state, as a result, it is important to consider every transition logic and the input required for these logic to be executed. A moore machine transition logic can be implemented on an FPGA with the statements below.

1. The input sequence $ain[1:0] = 01, 00$ causes the output to become 0.
2. The input sequence $ain[1:0] = 11, 00$ causes the output to become 1.
3. The input sequence $ain[1:0] = 10, 00$ causes the output to become toggle.

 


Figure 2.1: Moore state machine diagram for ain.

Figure 2.1 illustrates the required states for output. S4, S5 and S6 are the only states where the LED outputs may alter. In contrast, S1, S2 and S3 are buffer states. Additionally, S0 will be the initial state and output 0. Furthermore, these states and its corresponding output can be shown in Table 1. Previously mentioned states can be achieved with a provided input sequence "ain" such as 01, 11, 10. This design step is integral in developing an FSM as it simplifies the logic in great detail before implementation.

Current state	output
S0	0
S1	x
S2	x
S3	x
S4	0
S5	1
S6	Toggle

Table 1: Figure 2.1's states and corresponding outputs.

FSM implementation

Implementing the moore FSM requires 2 main processes, output decode logic, and transition logic. Additionally, states of these FSM will be declared as "type" to comply with the RTL architecture. Furthermore, "state" and "next_state" will be declared as signal, and "prev" signal was declared as a median to memorise the previous state output as shown in Figure 3.1

```

34 entity moore is
35     Port ( ain : in STD_LOGIC_VECTOR (1 downto 0);
36           clk : in STD_LOGIC; Reset : in STD_LOGIC;
37           m : inout STD_LOGIC);
38 end moore;
39
40 architecture Behavioral of moore is
41
42     type state_type is (S0, S1, S2, S3, S4, S5, S6);
43     signal state, next_state : state_type;
44     signal prev : STD_LOGIC := '0'; --previous state

```

Figure 3.1: Declaring moore states.

To transition to the 3 buffer states (S1, S2, S3), S0 must be the default FSM state. This will allow the S0 to transition to the buffer states based on the inputs provided in Table 1 to as shown in Figure 3.2. Consequently, for the buffer states to transition to the output states (S4, S5, S6) it will require a "00" input after reaching the buffer state; an example can be provided in Figure 3.3. This fits within the parameters of a moore machine as the output will only change based on the current state the machine is in e.g (S4 : 0, S5 : 1, S6 : toggle) as shown in Figure 3.4. However, the output state has the options to return back to buffer states or the default FSM as shown in Figure 3.5; following the logic in section 2.

```

when S0 =>
  if (ain = "01") then
    next_state <= S1;

  elsif (ain = "11") then
    next_state <= S2;

  elsif (ain = "10") then
    next_state <= S3;
  else
    next_state <= S0;
  end if;

```

Figure 3.2: Default state to buffer state transition logic.

```

when S3 =>
  if (ain = "01") then
    next_state <= S1;

  elsif (ain = "11") then
    next_state <= S2;

  elsif (ain = "10") then
    next_state <= S3;

  elsif (ain = "00") then
    next_state <= S6;
  else
    next_state <= S0;
  end if;

```

Figure 3.3: Buffer state to output state logic example (ain = "00").

```

61 OUTPUT_DECODE : process (state)
62 begin
63   m <= '0';
64   prev <= m;
65   case (state) is
66   when S4 =>
67     m <= '0';
68     prev <= m;
69   when S5 =>
70     m <= '1';
71     prev <= m;
72   when S6 =>
73     m <= not prev;
74     prev <= m;
75   when others =>
76     prev <= m;
77   end case;
78 end process;

```

Figure 3.4: Output decode state when the 3 output states are reached (S4 : 0, S5 : 1, S6 : T).

```

137 when S4 =>
138   if (ain = "01") then
139     next_state <= S1;
140
141   elsif (ain = "11") then
142     next_state <= S2;
143
144   elsif (ain = "10") then
145     next_state <= S3;
146
147   elsif (ain = "00") then
148     next_state <= S0;
149   else
150     next_state <= S4; -- else stays in this state
151   end if;

```

Figure 3.5: Output state to buffer state/default state logic example (lines 138 to 148).

FSM testbench

```

37 :
38 : architecture Behavioral of moore_tb is
39 : component moore is
40 :     Port ( ain : in STD_LOGIC_VECTOR (1 downto 0);
41 :           clk : in STD_LOGIC; Reset : in STD_LOGIC;
42 :           m : inout STD_LOGIC);
43 : end component;
44 :
45 : signal clock : std_logic := '0';
46 : signal r : std_logic := '0';
47 : signal input : std_logic_vector(1 downto 0) := "00";
48 : signal output : std_logic := '0';
49 : constant clk_period : time := 10ns;

```

Figure 4.1: Moore machine testbench declaration.

As shown in Figure 4.1, the test bench for this FSM was created and the FSM must be declared as a component to allow for instantiation. Consequently, signals must be declared to allow the testbench sequences to be inputted into the moore machine. Finally, the moore machine was instantiated and its inputs were routed to the previously declared signals as shown in figure 4.2.

```

53 : moore_instance: moore PORT MAP (
54 :     clk => clock,
55 :     Reset => r,
56 :     ain => input,
57 :     m => output
58 : );

```

Figure 4.2: Moore instance routed to testbench signals.

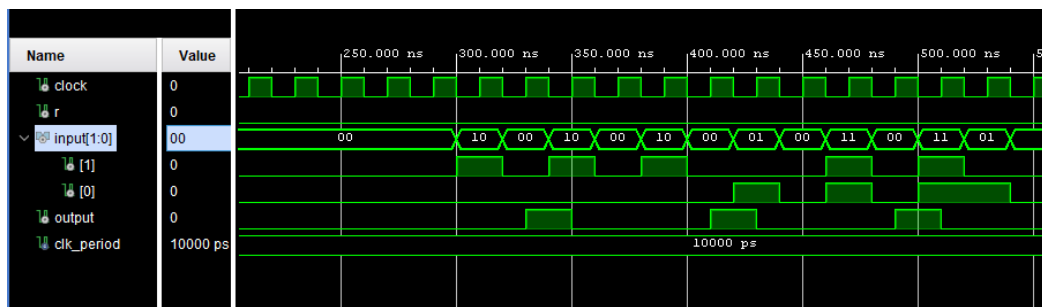


Figure 4.3: Testbench output of the moore machine.

As illustrated in Figure 4.3, the moore machine works as intended when given a set of input sequences (as shown in the appendix); its inputs are based on the logic stated in section 2. When ain = "11", followed by ain = "00", the LED outputs a 1. Additionally, the toggle state based on the previous output works accordingly (as shown between 300ns to 425ns in Figure 4.3).

Conclusion

In conclusion, the implementation of a moore FSM can be simplified with the use of diagrams and logic statements. Testbench is an important part of an FPGA circuit design as it allows developers to have an in-depth understanding of how the circuit design would react based on a set of automated inputs without the hassle of manual test cases. As section 4, the moore machine was quickly validated with the use of a testbench.

Appendix

```

34 entity moore is
35     Port ( ain : in STD_LOGIC_VECTOR (1 downto 0);
36           clk : in STD_LOGIC; Reset : in STD_LOGIC;
37           m : inout STD_LOGIC);
38 end moore;
39
40 architecture Behavioral of moore is
41
42     type state_type is (S0, S1, S2, S3, S4, S5, S6);
43     signal state, next_state : state_type;
44     signal prev : STD_LOGIC := '0'; --previous state
45
46
47     begin
48
49
50     SYNC_PROC : process (clk)
51     begin
52         if rising_edge(clk) then
53             if (reset = '1') then
54                 state <= S0;
55             else
56                 state <= next_state;
57             end if;
58         end if;
59     end process;
60
61
62     OUTPUT_DECODE : process (state)
63     begin
64         m <= '0';
65         prev <= m;
66         case (state) is
67             when S4 =>
68                 m <= '0';
69                 prev <= m;
70             when S5 =>
71                 m <= '1';
72                 prev <= m;
73             when S6 =>
74                 m <= not prev;
75                 prev <= m;
76             when others =>
77                 prev <= m;
78         end case;
79     end process;

```

```

80      NEXT_STATE_DECODE : process (state, ain)
81      begin
82          ○      next_state <= S0;
83      ○      case (state) is
84      ○          when S0 =>
85      ○              if (ain = "01") then
86      ○                  next_state <= S1;
87
88      ○              elsif (ain = "11") then
89      ○                  next_state <= S2;
90
91      ○              elsif (ain = "10") then
92      ○                  next_state <= S3;
93      ○              else
94      ○                  next_state <= S0;
95      ○              end if;
96      ○          when S1 =>
97      ○              if (ain = "01") then
98      ○                  next_state <= S1;
99
100      ○              elsif (ain = "11") then
101      ○                  next_state <= S2;
102
103      ○              elsif (ain = "10") then
104      ○                  next_state <= S3;
105
106      ○              elsif (ain = "00") then
107      ○                  next_state <= S4;
108      ○              end if;
109      ○          when S2 =>
110      ○              if (ain = "01") then
111      ○                  next_state <= S1;

```

112			
113	○		elsif (ain = "11") then
114	○		next_state <= S2;
115			
116	○		elsif (ain = "10") then
117	○		next_state <= S3;
118			
119	○		elsif (ain = "00") then
120	○		next_state <= S5;
121	⊖		end if;
122	⊖	when S3 =>	
123	⊖	○	if (ain = "01") then
124	○		next_state <= S1;
125			
126	○		elsif (ain = "11") then
127	○		next_state <= S2;
128			
129	○		elsif (ain = "10") then
130	○		next_state <= S3;
131			
132	○		elsif (ain = "00") then
133	○		next_state <= S6;
134			else
135	○		next_state <= S0;
136	⊖		end if;
137	⊖	when S4 =>	
138	⊖	○	if (ain = "01") then
139	○		next_state <= S1;
140			

```

140
141 ○ elif (ain = "11") then
142 ○ next_state <= S2;
143
144 ○ elif (ain = "10") then
145 ○ next_state <= S3;
146
147 ○ elif (ain = "00") then
148 ○ next_state <= S0;
149 else
150 ○ next_state <= S4; -- else stays in this state
151 ○ end if;
152 ○ when S5 =>
153 ○ if (ain = "01") then
154 ○ next_state <= S1;
155
156 ○ elif (ain = "11") then
157 ○ next_state <= S2;
158
159 ○ elif (ain = "10") then
160 ○ next_state <= S3;
161
162 ○ elif (ain = "00") then
163 ○ next_state <= S0;
164 else
165 ○ next_state <= S5; -- else stays in this state
166 ○ end if;
167 ○ when S6 =>
168 ○ if (ain = "01") then
169 ○ next_state <= S1;
170 ○ elif (ain = "11") then
171 ○ next_state <= S2;
172
173 ○ elif (ain = "10") then
174 ○ next_state <= S3;
175 ○ elif (ain = "00") then
176 ○ next_state <= S0;
177 else
178 ○ next_state <= S6; -- else stays in this state
179 ○ end if;
180 ○ when others =>
181 ○ next_state <= S0;
182 ○ end case;
183 end process;
184 end Behavioral;
185

```


Testbench

```
34 entity moore_tb is
35     -- Port ( );
36 end moore_tb;
37
38 architecture Behavioral of moore_tb is
39     component moore is
40         Port ( ain : in STD_LOGIC_VECTOR (1 downto 0);
41               clk : in STD_LOGIC; Reset : in STD_LOGIC;
42               m : inout STD_LOGIC);
43     end component;
44
45     signal clock : std_logic := '0';
46     signal r : std_logic := '0';
47     signal input : std_logic_vector(1 downto 0) := "00";
48     signal output : std_logic := '0';
49     constant clk_period : time := 10ns;
50
51     begin
52
53     moore_instance: moore PORT MAP (
54     clk => clock,
55     Reset => r,
56     ain => input,
57     m => output
58     );
59
```

```

61  ⊞ process
62      begin
63          ○ r <= '1';
64          ○ wait for 100ns;
65          ○ r <= '0';
66          ○ wait for 200ns;
67          ○ input <= "10";
68          ○ wait for 20ns;
69          ○ input <= "00"; -- test the 3rd condition (S3, S6)
70          ○ wait for 20ns;
71          ○ input <= "10";
72          ○ wait for 20ns;
73          ○ input <= "00"; -- test the 3rd condition (S3, S6)
74          ○ wait for 20ns;
75          ○ input <= "10";
76          ○ wait for 20ns;
77          ○ input <= "00"; -- test the 3rd condition (S3, S6)
78          ○ wait for 20ns;
79          ○ input <= "01";
80          ○ wait for 20ns;
81          ○ input <= "00"; -- test the 1st condition (S1, S4)
82          ○ wait for 20ns;
83          ○ input <= "11";
84          ○ wait for 20ns;
85          ○ input <= "00"; -- test the 2nd condition (S2, S5)
86          ○ wait for 20ns;
87          ○ input <= "11"; -- test jump conditions (S2 to S1)
88          ○ wait for 20ns;
89          ○ input <= "01";
90          ○ wait for 20ns;
91          ○ input <= "00"; -- test the 1st condition (S1, S4)
92          ○ wait for 20ns;
93          ○ wait;
94  ⊞ end process;
95
96  ○ clock <= not clock after clk_period;
97
98
99  ⊞ end Behavioral;

```